

**ECE 214 - Virtual Lab #10**  
**Thévenin Equivalent Circuits**  
**Modified for Analysis Only**

17 April 2020

**Introduction:** In this lab, you will examine the Thévenin equivalent output impedance of the DC-DC Power Supply designed in [Lab #9](#).

**Circuit Analysis:**

1. For the DC-DC Power Supply of [Lab #9](#), derive the equations for the Thévenin equivalent output impedance under the two operating conditions:
  - (a) Condition 1: the D and S terminals of the transistor in the Boost Converter are shorted. All of the current flowing through the inductor also flows through the transistor, and
  - (b) Condition 2: the D and S terminals of the transistor in the Boost Converter are open. All of the current flowing through the inductor flows onto the capacitor.
2. Plot on a semi-log graph:
  - (a) The magnitude of the Thévenin equivalent output impedance as a function of frequency for frequencies between 1 Hz and 1 MHz for both operating conditions.
  - (b) The phase angle of the Thévenin equivalent output impedance as a function of frequency for frequencies between 1 Hz and 1 MHz for both operating conditions.
3. Discuss the results of this analysis.