

ECE 214 — Make up Exam #1

Estimated time for completion: ≤ 1.25 hour
22 March 2017

Rules of the Exam


- Rule 1:** The examination period begins at 5:00pm on Wednesday 22 March 2017 and ends at 6:15am on Wednesday 22 March 2017.
- Rule 2:** The exam is 15% of your grade.
- Rule 3:** There are a total of 15 answers. Each answer is worth 1 point. Circle the most correct answer.
- Rule 4:** The exam is closed book and closed notes. You may use your ECE 214 Laboratory Notebook, a ruler, and a calculator.

Answer Key

Name

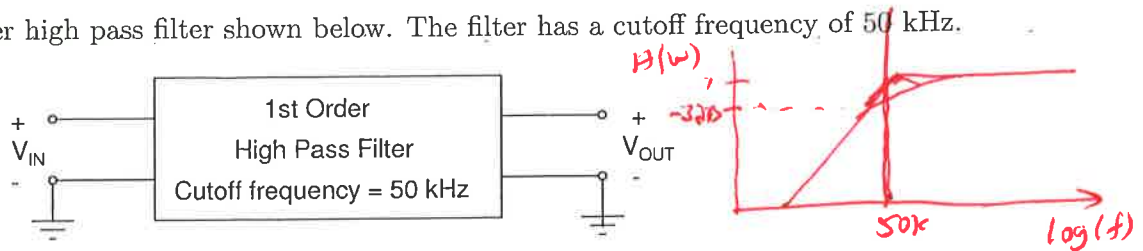Problem 1: 1st Order High Pass Filter

Consider the first order high pass filter shown below. The filter has a cutoff frequency of 50 kHz.



1. V_{IN} is a triangular wave with a 50% duty cycle and a frequency of 100 kHz. What is the relative amplitude of the 5th harmonic to the fundamental frequency at the output of the filter?

- (a) 0 dB
- (b) -3 dB
- (c) -11 dB
- (d) -14 dB
- (e) -17 dB
- (f) -21 dB
- ☒ (g) -28 dB
- (h) none of the above

$$20 \log\left(\frac{1}{5}\right)$$

100 kHz is in the passband

2. V_{IN} is a square wave with a 50% duty cycle and a frequency of 100 kHz. What is the relative amplitude of the 5th harmonic to the fundamental frequency at the output of the filter?

- (a) 0 dB
- (b) -3 dB
- (c) -11 dB
- ☒ (d) -14 dB
- (e) -17 dB
- (f) -21 dB
- (g) -28 dB
- (h) none of the above

$$20 \log\left(\frac{1}{5}\right)$$

100 kHz is in the passband

3. V_{IN} is a square wave with a 50% duty cycle and a frequency of 50 kHz. What is the relative amplitude of the 5th harmonic to the fundamental frequency at the output of the filter?

- (a) 0 dB
- (b) -3 dB
- ☒ (c) -11 dB
- (d) -14 dB
- (e) -17 dB
- (f) -21 dB
- (g) -28 dB
- (h) none of the above

$$-14 + 3 \text{ dB}$$

Fundamental attenuated by 3 dB

4. V_{IN} is a square wave with a 50% duty cycle and a frequency of 10 kHz. What is the relative amplitude of the 5th harmonic to the fundamental frequency at the output of the filter?

(a) 0 dB

(b) -3 dB

(c) -11 dB

(d) -14 dB

(e) -17 dB

(f) -21 dB

(g) -28 dB

(h) none of the above

Fundamental:
$$-\frac{20 \text{ dB}}{\text{decade}} \times \frac{\log(5)}{\log(10)} = -14 \text{ dB}$$

5th harmonic:
$$-3 \text{ dB}$$

Fundamental:
$$0 - 14 = -14$$

5th harmonic:
$$-14 - 3 = -17$$

$$17 = -3 \text{ dB}$$

5. V_{IN} is a square wave with a 50% duty cycle and a frequency of 1 kHz. What is the relative amplitude of the 3rd harmonic to the fundamental frequency at the output of the filter?

(a) 0 dB

(b) -3 dB

(c) -11 dB

(d) -14 dB

(e) -17 dB

(f) -21 dB

(g) -28 dB


(h) none of the above

Fundamental attenuated by -9.54 dB by filter
 and is at the same voltage level as

3rd harmonic

difference between fundamental & 3rd harmonic = 0 dB

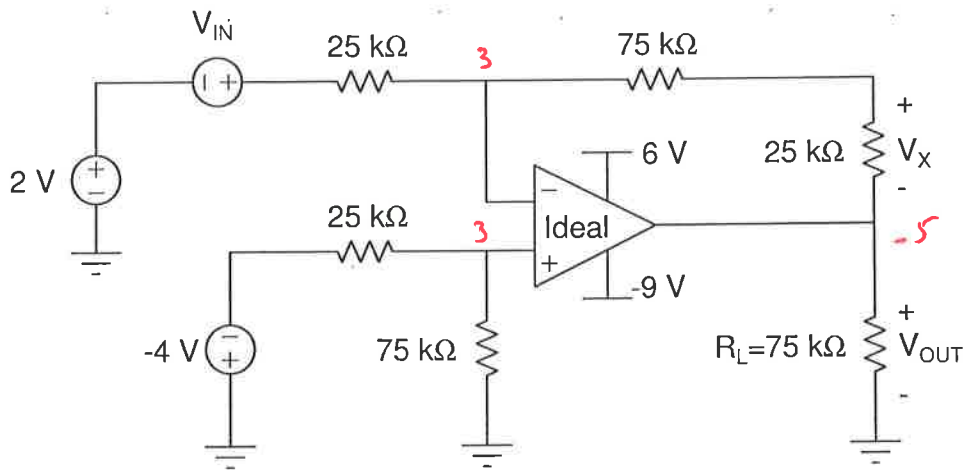Problem 2: Consider the OpAmp circuit below. The OpAmp is ideal.



1. When $V_{IN} = 0$ V what is the value of V_{OUT} ?

- (a) -9 V
- (b) -5 V
- (c) -2 V
- (d) 0 V
- (e) +2 V
- ☒ (f) +6 V *← Saturated*
- (g) None of the above

$$\frac{V_{in} + 2 - 3}{25} = \frac{3 - V_{out}}{75}$$

$$4(V_{in} - 1) = 3 - V_{out}$$

$$V_{out} = 7 - 4V_{in}$$

2. When $V_{IN} = +8$ V what is the value of V_{OUT} ?

- ☒ (a) -9 V *← Saturated*
- (b) -5 V
- (c) -2 V
- (d) 0 V
- (e) +2 V
- (f) +6 V
- (g) None of the above

3. When $V_{IN} = +3$ V what is the value of V_{OUT} ?

- (a) -9 V
- (b) -5 V
- (c) -2 V
- (d) 0 V
- (e) +2 V
- (f) +6 V
- (g) None of the above

$$V_{out} = 7 - 4V_{in}$$


4. If $V_{IN} = +3$ V and the resistance R_L is increased by 10X, how does V_{OUT} change?

- (a) V_{OUT} increases by 2.5X
- (b) V_{OUT} increases by more than 2.5X
- (c) V_{OUT} decreases by 2.5X
- (d) V_{OUT} decreases by more than 2.5X
- (e) V_{OUT} stays the same
- (f) None of the above

V_{out} does not depend on R_L


5. When $V_{IN} = +3$ V what is the value of V_X ?

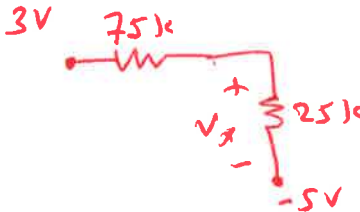- (a) -9 V
- (b) -5 V
- (c) -2 V
- (d) 0 V
- (e) +2 V
- (f) +6 V
- (g) None of the above



$$V_x = \frac{1}{4} \times 8 = 2V$$

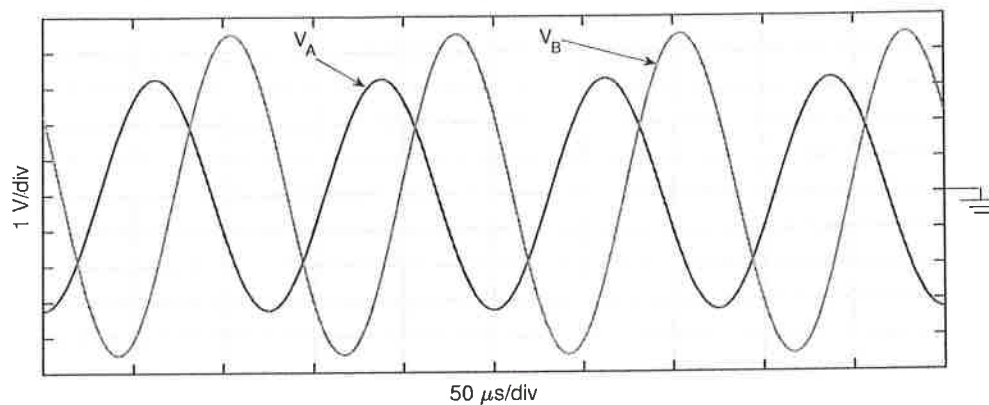Problem 3: Consider the oscilloscope trace shown below. Signal V_A is the input to an amplifier and V_B is the output from an amplifier.



The two sinusoidal signals can be represented by:

$$V_A(t) = A \cos(\omega t + \phi_1)V$$

and

$$V_B(t) = B \cos(\omega t + \phi_2)V$$

1. What is the gain of the amplifier?

- (a) 1.4
- (b) 2.8
- (c) 4.2
- (d) 5.6
- (e) None of the above

2. What is ω ?

- (a) 2k rad/s
- (b) 4k rad/s
- (c) 8k rad/s
- (d) 25k rad/s
- (e) 50k rad/s
- (f) none of the above

3. Which of the following statements best describes the phase shift between V_A and V_B ?
- (a) V_A leads V_B by 60°
 - (b) V_A lags V_B by 60°
 - (c) V_A leads V_B by 120°
 - (d) V_A lags V_B by 120°
 - (e) V_A lags V_B on the positive cycle and V_A leads V_B on the negative cycle
4. What is A?
- (a) 2.3 V
 - (b) 3.2 V
 - (c) 4.5 V
 - (d) 6.4 V
 - (e) 9.0 V
5. If the voltage A is measured on a DVM set to measure an AC voltage, what value would it read?
- (a) 2.3 V
 - (b) 3.2 V
 - (c) 4.5 V
 - (d) 6.4 V
 - (e) 9.0 V
- $\frac{3.2}{\sqrt{2}}$