

ECE 214 - Lab #3 — Filter Design

15 February 2021

Introduction

In this lab, you will design, simulate, build, and test a low-pass filter. The block diagram of the filter is shown in **Figure 1**.

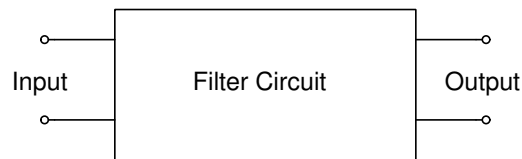


Figure 1: Block diagram of the filter circuit.

The filter circuit should satisfy the following specifications.

1. Input: Square wave with a frequency of 1.25 kHz and a peak-to-peak voltage of 4 V.
2. Output: Peak-to-peak voltage greater than 2 V and magnitude of the third harmonic at least -20 dB below the fundamental frequency.

These specifications are illustrated by the signals in **Figure 2**.

Parts List

The values and number of resistors and capacitors are dependent on the design.

Pre-Lab

1. Design a low-pass filter that satisfies the above specification.
2. Simulate the filter with a square wave input signal with a frequency of 1.25 kHz and a peak-to-peak voltage of 4 V, and verify that the signal at the output of the filter satisfies the specification. The MATLAB® file ECE214_2021_Lab3.m for NGspice is available at https://ece214.davidkotecki.com/docs/Matlab/ECE214_2021_Lab3.m. The MATLAB® function vt_to_vf, available at https://ece214.davidkotecki.com/docs/Matlab/vt_to_vf.m, is needed to approximate the Fourier series of the time-domain signals, and should be placed in the same directory as the ECE214_2020_Lab3.m file.
3. Plot the voltage at the input of the filter, and the output of the filter, as a function of time.
4. Plot the voltage at the input of the filter, and the output of the filter, as a function of frequency. Show the voltages in dB.

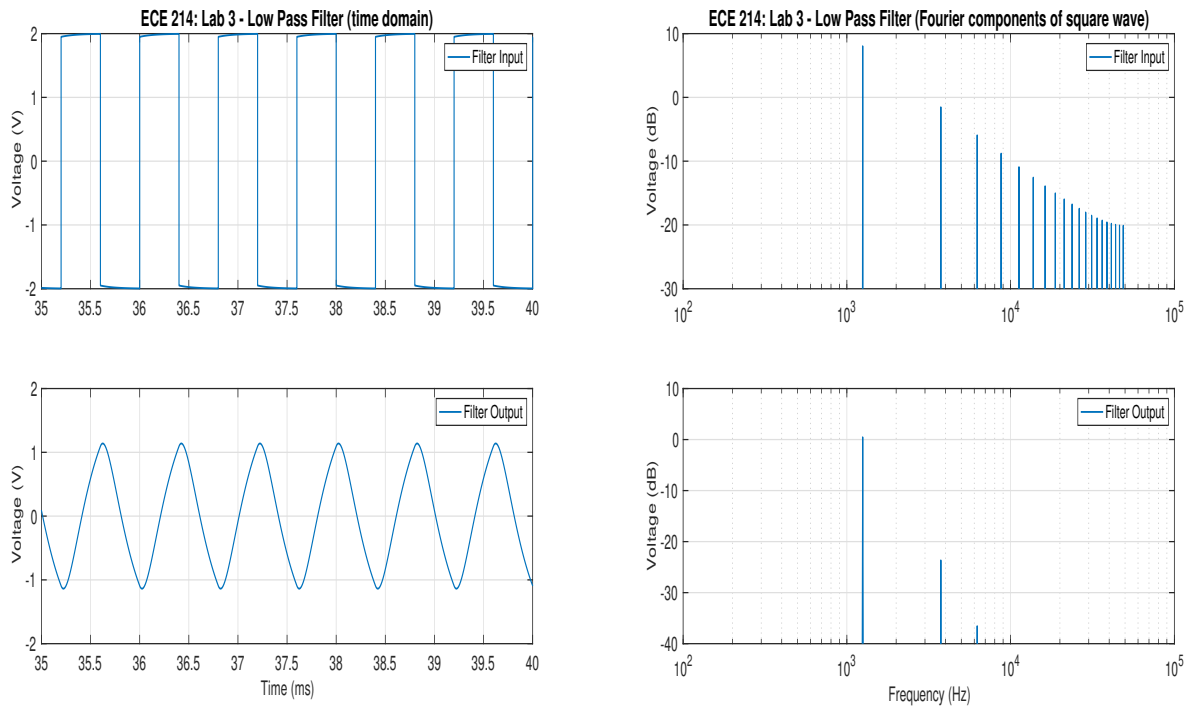


Figure 2: Low pass filter input signal (top) and output signal (bottom) in the time domain (left) and the frequency domain (right).

Lab Procedure

1. Build the filter designed in the Pre-Lab.
2. Connect the WG to the input of the filter. Set the WG to produce a 4 V peak-to-peak square wave signal at a frequency of 1.25 kHz. Capture the input and output signals on the scope. Use MATLAB® to plot the input and output signals in both the time-domain and the frequency-domain. Make sure all axes and peaks are properly labeled.
3. Does the output of the filter meet the specifications?
 - (a) If “Yes” you are done with the Lab Procedure.
 - (b) If “No” repeat this lab starting at step 1 in the Pre-Lab.

Post-Lab

1. Compare the measured results with the simulated results. Make a note of any discrepancies between the measurements and simulations.
2. In addition to the transient simulation, useful information on the response of a filter can be obtained using AC, or small signal, simulations. AC simulations are similar to Phasor

analysis. During AC simulations, the circuit response is simulated as a function of frequency. To learn more about AC and transient simulations, you should read Sections 1.2.2, 15.3.1 and 15.3.9 of the NGspice user manual <http://ngspice.sourceforge.net/docs/ngspice-manual.pdf>.

3. Simulate the frequency response of the circuit using AC simulation. (Uncomment the last sections of the ECE214_2021_Lab3.m MATLAB® file to enable the AC simulation.)
 - (a) Set the AC Voltage of the pulse generator in your schematic to 1 V. The AC Voltage is the magnitude of the voltage used when performing AC simulations.
 - (b) For AC simulations, the frequency variable in the NGspice data file is called FREQUENCY.
 - (c) By adding the `.ac dec 201 1e2 1e5` control statement in your .m file, the simulation will perform a frequency sweep containing of 201 frequency values ranging from 100 Hz to 100,000 Hz using a logarithmic scale.
 - (d) Plot the magnitude of the output voltage V_{out} in decibels as a function of frequency. To convert the output voltage to dB, use: `20.*log10(abs(Vout))`.
 - (e) Plot the phase of the output voltage V_{out} in degrees as a function of frequency. To convert the output voltage to phase, use: `angle(Vout).*180/pi`.
4. Compare the time domain simulations in Pre-Lab Section #2, to the AC simulations in Post-Lab Section #3. Explain the relationship between these two types of simulations. Do the time domain and frequency domain simulation results provide the same information? Are the results from the two types of simulations consistent?