

## ECE 214 — Exam #1

Estimated time for completion:  $\leq 1.25$  hour  
28 February 2018

### Rules of the Exam


- Rule 1:** The examination period begins at 9:30am on Tuesday 28 February 2017 and ends at 10:45am on Tuesday 28 February 2017.
- Rule 2:** The exam is 15% of your grade.
- Rule 3:** There are a total of 15 answers. Each answer is worth 1 point. Circle the most correct answer.
- Rule 4:** The exam is closed book and closed notes. You may use your ECE 214 Laboratory Notebook, a ruler, and a calculator.

Answer Key

\_\_\_\_\_  
Name
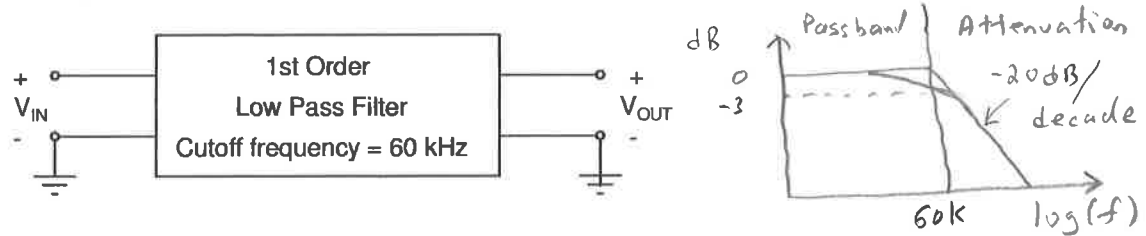
### Problem 1: 1st Order Low Pass Filter

Consider the first order low pass filter shown below. The filter has a cutoff frequency of 60 kHz.



1.  $V_{IN}$  is a sinusoidal waveform with a frequency of 10 kHz. What is the relative amplitude of the 3rd harmonic to the fundamental frequency at the output of the filter?

- (a) 0 dB
- (b) -3 dB
- (c) -6.5 dB
- (d) -9.5 dB
- (e) -12.4 dB
- (f) -16.1 dB
- (g) -19.1 dB

(h) none of the above

sinusoidal signals do not have any harmonics

2.  $V_{IN}$  is a square wave with a 50% duty cycle and a frequency of 10 kHz. What is the relative amplitude of the 3rd harmonic to the fundamental frequency at the output of the filter?

- (a) 0 dB
- (b) -3.0 dB
- (c) -6.5 dB
- (d) -9.5 dB
- (e) -12.4 dB
- (f) -16.1 dB
- (g) -19.1 dB

(h) none of the above

Both fundamental (10kHz) and 3rd harmonic are in the passband of the filter.  
For a square wave, 3rd harmonic is  $\frac{1}{3}$  amplitude of the fundamental

$$20 \log\left(\frac{1}{3}\right) = -9.54 \text{ dB}$$

3.  $V_{IN}$  is a square wave with a 50% duty cycle and a frequency of 20 kHz. What is the relative amplitude of the 3rd harmonic to the fundamental frequency at the output of the filter?

- (a) 0 dB
- (b) -3.0 dB
- (c) -6.5 dB
- (d) -9.5 dB
- (e) -12.4 dB
- (f) -16.1 dB
- (g) -19.1 dB

(h) none of the above

Fundamental (20kHz) is in the passband, 3rd harmonic is at the cutoff frequency and attenuated by -3 dB

$$\frac{\text{3rd harmonic}}{\text{fundamental}} = -9.54 - 3 = -12.54 \text{ dB}$$

4.  $V_{IN}$  is a square wave with a 50% duty cycle and a frequency of 60 kHz. What is the relative amplitude of the 3rd harmonic to the fundamental frequency at the output of the filter?

(a) 0 dB

(b) -3.0 dB

(c) -6.5 dB

(d) -9.5 dB

(e) -12.4 dB

(f) -16.1 dB

(g) -19.1 dB

(h) none of the above

Fundamental is attenuated by -3 dB

3rd harmonic is attenuated by -20 dB/decade

$$\hookrightarrow \frac{\log(3)}{\log(10)} \text{ of a decade} = 0.477 \text{ of a decade}$$

$$\frac{-20 \text{ dB}}{\text{decade}} \times 0.477 = -9.54 \text{ dB}$$

$$\frac{\text{3rd harmonic}}{-9.54 - 9.54} = -19.1 \text{ dB}$$

$$-19.1 \text{ dB} - (-3 \text{ dB})$$



5.  $V_{IN}$  is a square wave with a 50% duty cycle and a frequency of 80 kHz. What is the relative amplitude of the 3rd harmonic to the fundamental frequency at the output of the filter?

(a) 0 dB

(b) -3.0 dB

(c) -6.5 dB

(d) -9.5 dB

(e) -12.4 dB


(f) -16.1 dB

(g) -19.1 dB

(h) none of the above


Both fundamental and 3rd harmonic  
on -20 dB/decade slope

$$-19.54 - 19.54 = -39.08 \text{ dB}$$

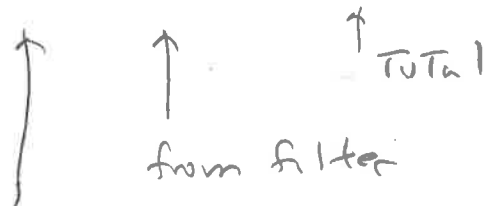

Square wave

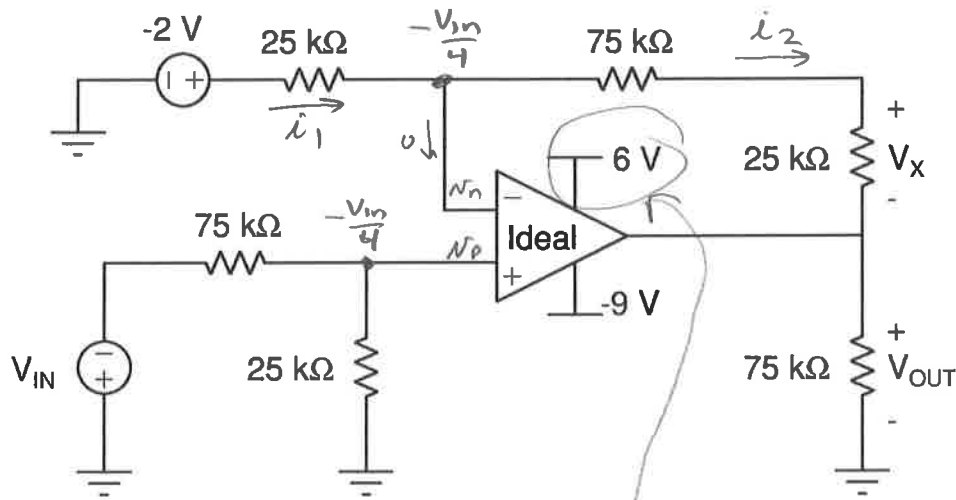**Problem 2:** Consider the OpAmp circuit below. The OpAmp is ideal.



1. Which of the following best describes this amplifier circuit?

- (a) inverting amplifier with a dc offset
- (b) non-inverting amplifier with a dc offset
- (c) inverting integrator with a dc offset
- (d) non-inverting integrator with a dc offset
- (e) Schmitt trigger
- (f) None of the above

2. When  $V_{IN} = 0$  V what is the value of  $V_{OUT}$ ?

- (a) -9 V
- (b) -6 V
- (c) -2 V
- (d) 0 V
- (e) +2 V
- (f) +6 V
- (g) None of the above

$$i_1 = i_2$$

$$\text{KCL @ } N_n$$

$$\frac{-2 - (-\frac{V_{in}}{4})}{25k} = \frac{-\frac{V_{in}}{4} - V_{out}}{100k}$$

$$-8 + V_{in} = -\frac{V_{in}}{4} - V_{out}$$

$$V_{out} = 8 - \frac{5V_{in}}{4}$$

Inverting amplifier  
DC offset

$$V_{in} = 0 \Rightarrow V_{out} = 8V$$

However, saturation voltage  
is 6 V

3. When  $V_{IN} = 8\text{ V}$  what is the value of  $V_{OUT}$ ?

(a) -9 V

(b) -6 V

(c) -2 V

(d) 0 V

(e) +2 V

(f) +6 V

(g) None of the above

$$V_{OUT} = 8 - \frac{5}{4} \times 8 = -2\text{ V}$$

4. When  $V_{IN} = 8\text{ V}$  what is the value of  $V_X$ ?

(a) -9 V

(b) -6 V

(c) -2 V

(d) 0 V

(e) +2 V

(f) +6 V

(g) None of the above

$$\begin{aligned} \text{Since } V_n &= V_{OUT} & V_2 &= 0 \\ \text{and } V_x &= 0 \end{aligned}$$

5. If the ideal OpAmp in this circuit is replaced with a TL082 OpAmp, what would you expect for the maximum obtainable output voltage?

(a) +5 V

(b) +6 V


(c) +8 V

(d) +9 V

(e) +11 V

From Lab #4: About 1V lower than the supply voltage

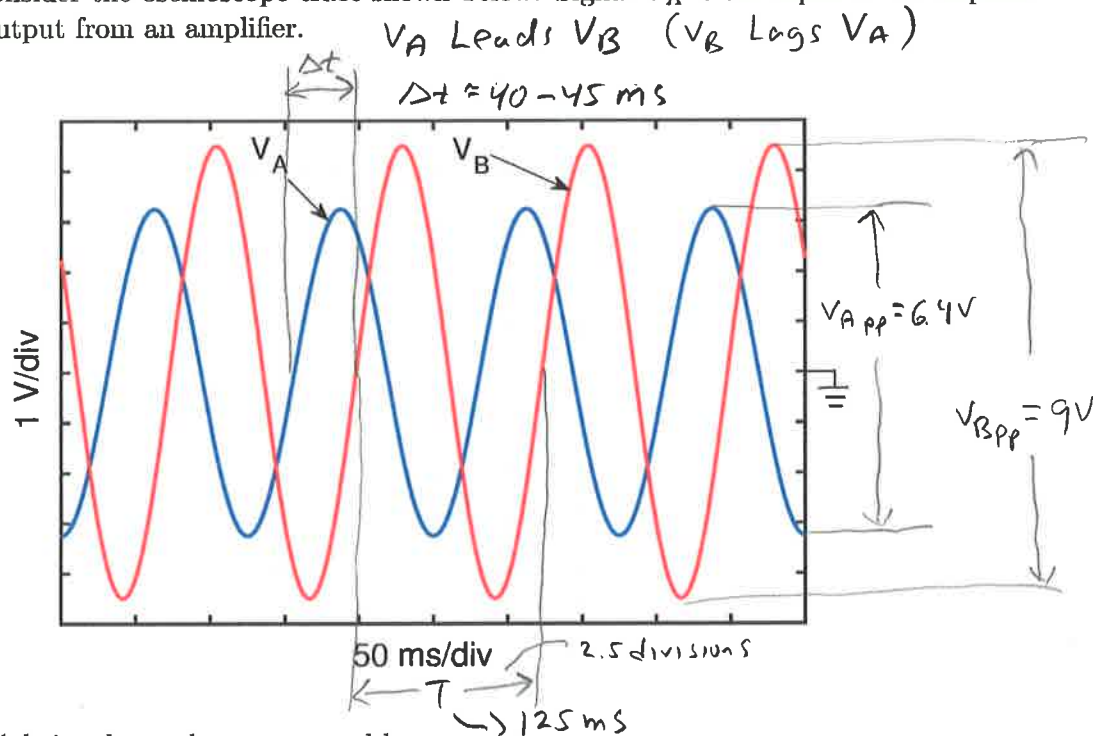**Problem 3:** Consider the oscilloscope trace shown below. Signal  $V_A$  is the input to an amplifier and  $V_B$  is the output from an amplifier.



The two sinusoidal signals can be represented by:

$$V_A(t) = A \cos(\omega t + \phi_1) \text{ V}$$

and

$$V_B(t) = B \cos(\omega t + \phi_2) \text{ V}$$

1. What is the gain of the amplifier?

(a) 1.4

(b) 2.8

(c) 4.2

(d) 5.6

(e) None of the above

$$\frac{9 \text{ V}}{6.4 \text{ V}}$$

2. What is  $\omega$ ?

(a) 2k rad/s

(b) 4k rad/s

(c) 8k rad/s

(d) 25k rad/s

(e) 50k rad/s

(f) none of the above

$$\omega = 2\pi f = \frac{2\pi}{T} = 50 \text{ rad/s}$$

3. Which of the following statements best describes the phase shift between  $V_A$  and  $V_B$ ?

(a)  $V_A$  lags  $V_B$  by  $60^\circ$

(b)  $V_A$  leads  $V_B$  by  $60^\circ$

(c)  $V_A$  lags  $V_B$  by  $120^\circ$

(d)  $V_A$  leads  $V_B$  by  $120^\circ$

(e)  $V_A$  lags  $V_B$  on the positive cycle and  $V_A$  leads  $V_B$  on the negative cycle

$V_A$  Leads  $V_B$

$$\theta_{ps} = \frac{\Delta t}{T} \times 360^\circ$$

$$\left\{ \begin{array}{l} \frac{40ms}{125ms} \times 360^\circ = 115^\circ \\ \frac{45ms}{125ms} \times 360^\circ = 130^\circ \end{array} \right.$$

4. What is B?

(a) 2.3 V

(b) 3.2 V

(c) 4.5 V

(d) 6.4 V

(e) 9.0 V

$$V_B = \frac{V_{B_{pp}}}{2} = \frac{9V}{2} = 4.5V$$

5. If the voltage B is measured on a DVM set to measure an AC voltage, what value would it read?

(a) 2.3 V

(b) 3.2 V

(c) 4.5 V

(d) 6.4 V

(e) 9.0 V

$\overline{L}$  measures rms voltage

$$V_{B_{rms}} = \frac{4.5}{\sqrt{2}} = 3.2V$$