

ECE 214 — Exam #2

Estimated time for completion: ≤ 1.25 hour
24 April 2018


Rules of the Exam

- Rule 1:** The examination period begins at 11:00 am on Tuesday, 24 April 2018 and ends at 12:15 pm on Tuesday, 24 April 2018.
- Rule 2:** The exam is worth 15 points.
- Rule 3:** There are three problems, and each problem is worth 6 points. The maximum score is 18 out of 15.
- Rule 4:** The exam is closed book and closed notes. You may use your ECE 214 Laboratory Notebook, a ruler, and a calculator.
- Rule 5:** To receive credit for an answer include the units along with the numerical answer.
- Rule 6:** Show all work - answers without supporting work will not receive credit.
- Rule 7:** Do not leave the room until you have completed the exam.

Answer Key

Name

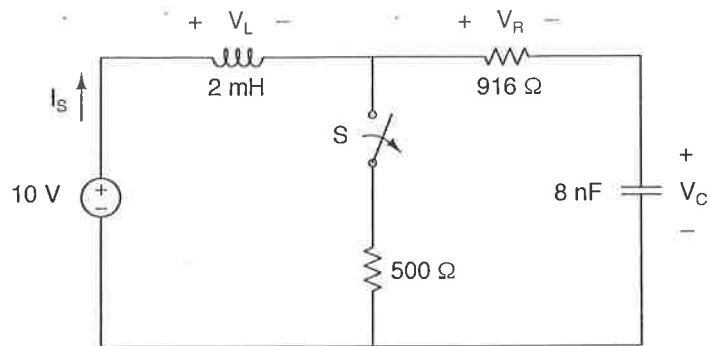Problem 1: In the circuit below, switch S has been closed for a long time and then opens at $t = 0$.



Complete the table on page 3, and derive the equation describing $V_C(t)$ for $t \geq 0$.

	$t = 0^-$	$t = 0^+$	$t = \infty$
I_S	20 mA	→ 20 mA	0
V_L	0	-18.32 V	0
V_R	0	18.32 V	0
V_C	10 V	→ 10 V	10 V

What is the equation for $V_C(t)$ for $t \geq 0$?

$$V_C(t) = 24.9 e^{-\alpha t} \sin(\omega_d t) + 10$$

$$\alpha = \frac{R}{2L} = \frac{916}{4 \times 10^{-3}} = 229,000 \text{ rad/s}$$

$$\omega_0 = (LC)^{-1/2} = 250,000 \text{ rad/s}$$

$\alpha < \omega_0$ Underdamped

$$\omega_d = (\omega_0^2 - \alpha^2)^{1/2} = 100,249 \text{ rad/s}$$

$$V_C(t) = A_1 e^{-\alpha t} \cos(\omega_d t) + A_2 e^{-\alpha t} \sin(\omega_d t) + V_C(\infty)$$

$$V_C(0) = 10 = A_1 + 10 \Rightarrow A_1 = 0$$


$$V_C(t) = A_2 e^{-\alpha t} \sin(\omega_d t) + 10 \text{ V}$$

$$C \left. \frac{dV_C}{dt} \right|_{t=0} = i(0) = 20 \times 10^{-3} = 8 \times 10^{-9} A_2 [\omega_d]$$

$$A_2 = \frac{i(0)}{\omega_d C} = \frac{20 \times 10^{-3}}{\omega_d C} = 24.9$$

$$A_2 = 24.9$$


Problem 2: Consider the circuit below:

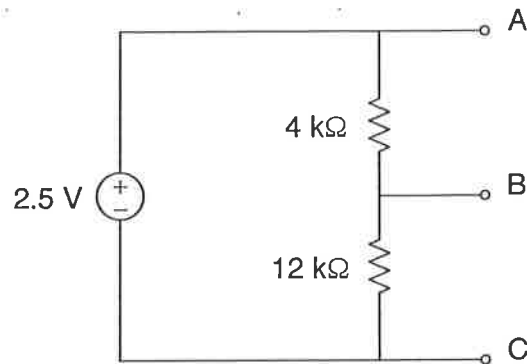

- a) Draw the Thévenin equivalent circuit representing terminals A and B.

$$V_{TH} = 2.5 \times \frac{4}{16}$$


$$R_{TH} = 4 // 12 = 3k$$

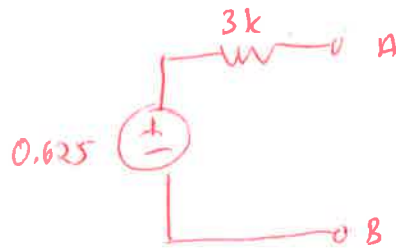

- b) Draw the Thévenin equivalent circuit representing terminals A and C.

$$V_{TH} = 2.5 V$$


$$R_{TH} = 0$$

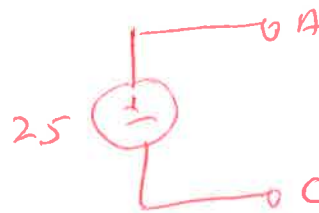


- c) Draw the Thévenin equivalent circuit representing terminals B and C.

$$V_{TH} = 2.5 \times \frac{12}{16}$$

$$R_{TH} = 4 // 12 = 3k$$

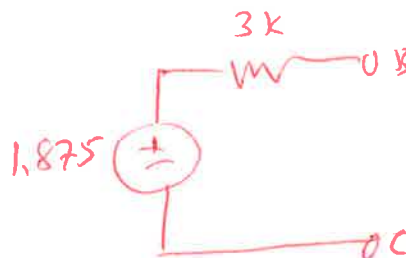

Problem 3: Consider the circuit below:

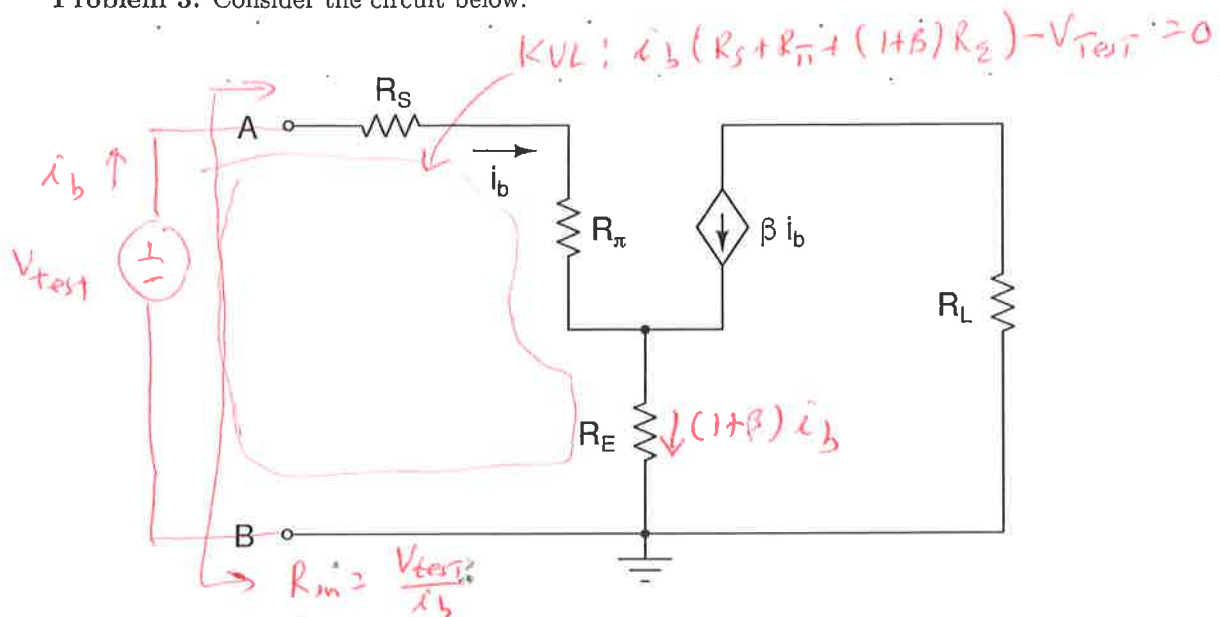

Part A: When $R_E = 0\Omega$, $R_S = R_{\pi} = R_L = 10\Omega$, and $\beta = 99$, what is the equivalent resistance between terminals A and B?

20 Ω

Part B: When $R_S = 0\Omega$, $R_E = R_{\pi} = R_L = 10\Omega$ and $\beta = 99$, what is the equivalent resistance between terminals A and B?

1010 Ω

Part C: When $R_E = R_S = R_{\pi} = R_L = 10\Omega$ and $\beta = 99$, what is the equivalent resistance between terminals A and B?

1020 Ω

$$R_{in} = \frac{V_{test}}{i_b} = R_S + R_{\pi} + (1+\beta)R_E$$

Blank page for calculations.

Name: _____

Blank page for calculations.

Name: _____