

## ECE 214 - Virtual Lab #10 Thévenin Equivalent Circuits Modified for Analysis Only

17 April 2020

**Introduction:** In this lab, you will examine the Thévenin equivalent output impedance of the DC-DC Power Supply designed in [Lab #9](#).

### Circuit Analysis:

1. For the DC-DC Power Supply of [Lab #9](#), derive the equations for the Thévenin equivalent output impedance under each of the two operating conditions below.
  - (a) Condition 1: the D and S terminals of the transistor in the Boost Converter are shorted. All of the current flowing through the inductor also flows through the transistor.
  - (b) Condition 2: the D and S terminals of the transistor in the Boost Converter are open. All of the current flowing through the inductor flows onto the capacitor.
2. Plot the following on a semi-log graph.
  - (a) The magnitude of the Thévenin equivalent output impedance as a function of frequency for frequencies between 1 Hz and 1 MHz for both operating conditions described in [step 1](#).
  - (b) The phase angle of the Thévenin equivalent output impedance as a function of frequency for frequencies between 1 Hz and 1 MHz for both operating conditions described in [step 1](#).
3. Discuss the results of this analysis.