

## ECE 214 - Lab #5

### OpAmp Circuits with Positive Feedback

24 February 2020

**Introduction:** Two LM741 Operational Amplifiers (OpAmps) are used to produce an oscillator. A system level block diagram is shown in **Figure 1**. The oscillator is formed by connecting the output of a Schmitt trigger, shown in **Figure 2**, to the input of an inverting integrator, and then connecting the output of the inverting integrator back to the input of the Schmitt trigger. The oscillator circuit is shown in **Figure 3**. The input to the circuit is a DC voltage of  $+V_{SUP}$ . The output of the circuit consists of a  $\sim 10 V_{pp}$  square wave and a  $\sim 5 V_{pp}$  triangular wave .

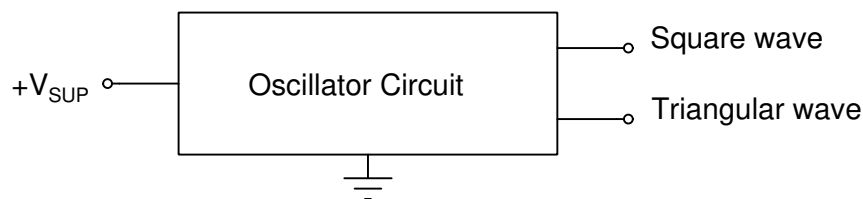


Figure 1: Block diagram of the oscillator circuit.

#### Circuit Specification:

1. Input:  $+V_{SUP} = 12 \text{ V DC}$
2. Outputs:
  - (a) Square wave ( $\sim 10 V_{pp}$ )
  - (b) Triangular wave ( $5 \pm 0.2 V_{pp}$ )
  - (c) Frequency =  $5.0 \pm 0.2 \text{ kHz}$
  - (d) Duty cycle =  $50 \pm 2\%$

#### Pre-Lab:

1. There are many ways to implement a Schmitt trigger. One method uses an OpAmp configured with positive feedback as shown in **Figures 2(a)** and **2(b)** for the dual-rail and single-rail OpAmp configuration, respectively. In both of these circuits, the output of the OpAmp ( $V_{OUT}$ ) is connected through resistor  $R_2$  to the **non-inverting** input ( $v_p$ ) of the OpAmp. This results in an amplifier circuit with positive feedback.

When an OpAmp is configured with positive feedback:  $v_p \neq v_n$ . Rather  $V_{out}$  takes on one of only two values:  $+V_{SUP}$  or  $-V_{SUP}$ . The output voltage  $V_{OUT} = +V_{SUP}$  when  $v_p > v_n$ , and  $V_{OUT} = -V_{SUP}$  when  $v_p < v_n$ .  $V_{OUT}$  transitions between  $-V_{SUP}$  and  $+V_{SUP}$  when  $v_p = v_n$ . The input voltages  $V_{IN}$  which cause the output to switch between  $-V_{SUP}$  and  $+V_{SUP}$ , and between  $+V_{SUP}$  and  $-V_{SUP}$  are known as the trigger levels.

Assume the OpAmp in **Figure 2(b)** is ideal. Analyze this circuit and derive an equation for the two trigger levels in terms of the resistor values  $R_1$  and  $R_2$ . When  $R_1 = 3 \text{ k}\Omega$  and  $R_2 = 12 \text{ k}\Omega$ ,

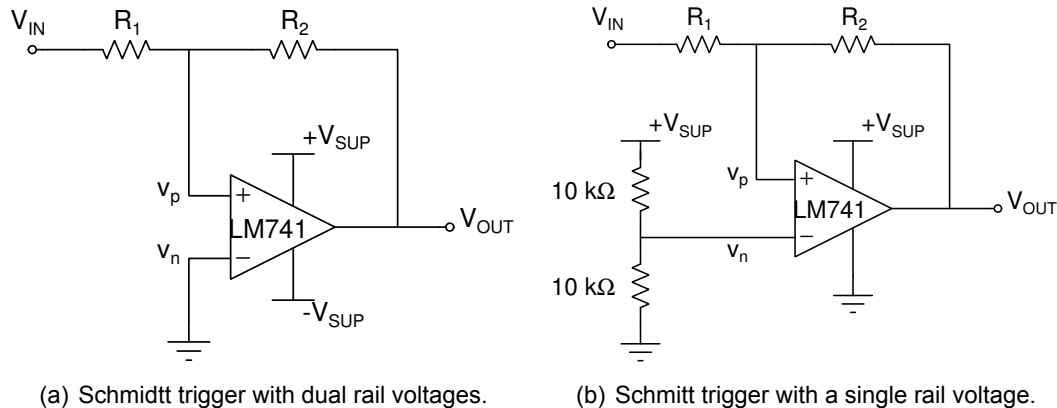


Figure 2: Schmitt trigger circuit using an Op Amp with positive feedback.

calculate the trigger levels that cause the output to switch from zero to  $+V_{SUP}$ , and from  $+V_{SUP}$  to zero, and

- Sketch the transfer function as  $V_{IN}$  increases from 0 V to  $+V_{SUP}$  V.
- Sketch the transfer function as  $V_{IN}$  decreases from  $+V_{SUP}$  V to 0 V.

Make sure the two trigger levels are labeled on the sketch.

- For the Schmitt trigger circuit in **Figure 2(b)**, determine values for resistors  $R_1$  and  $R_2$  so that the separation of the Schmitt trigger levels are  $5 \pm 0.2$  V. Assume the OpAmp is ideal and  $+V_{SUP} = 12$  V. With the chosen values of  $R_1$  and  $R_2$ , what are the two Schmitt trigger levels?
- Simulate the transfer function of the Schmitt trigger circuit in **Figure 2(b)** with the resistor values you calculated in step 2. Set the power supply voltage ( $+V_{SUP}$ ) to 12 VDC, and set the input voltage ( $V_{IN}$ ) to a DC voltage source. Use DC analysis to sweep the input voltage between 0 to 12 V. A MATLAB® file for NGspice is available at [https://ece214.davidkotecki.com/docs/Matlab/ECE214\\_2020\\_Lab5\\_Schmitt.m](https://ece214.davidkotecki.com/docs/Matlab/ECE214_2020_Lab5_Schmitt.m). Analyze the simulated behavior of the circuit using the ideal OpAmp and the LM741 OpAmp.
  - Simulate the output voltage as the input voltage is increased from 0 V to 12 V.
  - Simulate the output voltage as the input voltage is decreased from 12 V to 0 V.
  - What are the trigger levels for the Ideal and LM741 OpAmps.?
  - How does the LM741 OpAmp compare with an ideal OpAmp?

Make sure all axes on your graphs are properly labeled.

- Do the simulated results for the LM741 OpAmp meet the requirement that the trigger levels are separated by  $5 \pm 0.2$  V? If not, adjust the values of  $R_1$  and  $R_2$  so that the trigger levels meet this requirement. Record the final values of  $R_1$  and  $R_2$  in your notebook.
- Describe the function of the circuit shown in **Figure 3**. Assume the variable resistor is set to the mid-point resistance. Sketch the shape of the expected output signals  $V_{OUT_1}$  and  $V_{OUT_2}$  as a function of time.

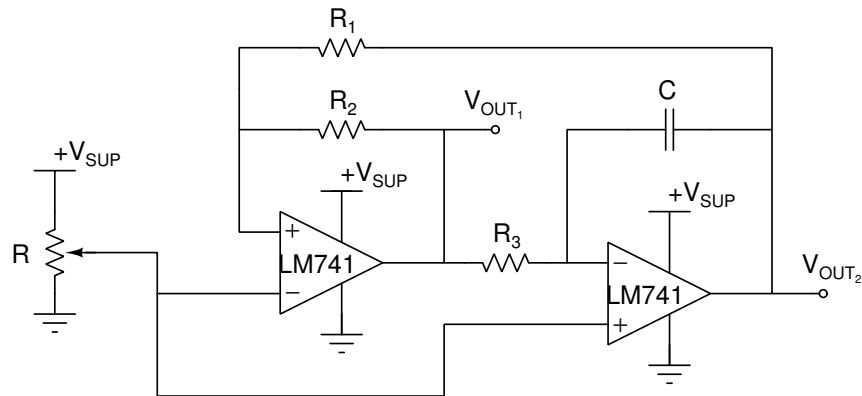


Figure 3: Oscillator circuit using a Schmitt trigger and an inverting integrator.

6. Assume the OpAmps are ideal. Derive the formula that relates the oscillation frequency to the values of the components  $R_1$ ,  $R_2$ ,  $R_3$ , and  $C$ . Make an entry in the table of contents indicating the page where the derivation and formula are located.
7. With  $C = 0.1 \mu\text{F}$ ,  $+V_{\text{SUP}} = 12 \text{ V}$ , and the variable resistor set at the mid-point, use the formula from [step 6](#), and the values of  $R_1$  and  $R_2$  determined in [step 2](#), to determine the value of  $R_3$  needed to produce an oscillation frequency of 5 kHz.

8. Perform a transient simulation of the circuit of [Figure 3](#) using the Ideal OpAmp. What is the simulated value of the oscillation frequency? What is the duty cycle? A MATLAB® file for NGSpice is available at [https://ece214.davidkotecki.com/docs/Matlab/ECE214\\_2020\\_Lab5\\_Osc.m](https://ece214.davidkotecki.com/docs/Matlab/ECE214_2020_Lab5_Osc.m).

For the transient simulation, an “initial condition (ic)” is added to ensure that the oscillator starts properly. The following line of code sets the initial condition:

```
.ic v(out1)=5
```

where out1 is the name of the output node of the Schmitt trigger.

9. Perform a transient simulation of the circuit of [Figure 3](#) using the LM741 OpAmp. Since the OpAmp is not ideal, the value of  $R_3$  you calculated may be off by as much as 20%. Adjust the value of  $R_3$ , if needed, to produce an oscillation frequency of  $5 \pm 0.2 \text{ kHz}$ .
10. Since the saturation voltages of the opamp are not 0 V and 12 V, the duty cycle of the waveform may not be 50%. If this is the case, adjust the reference voltage produced by the variable resistor to produce a  $50 \pm 2\%$  duty cycle. You may also have to readjust the value of  $R_3$  to keep the frequency in the range of  $5 \pm 0.2 \text{ kHz}$ .
11. Record in your notebook the final schematic of your oscillator circuit, listing all of the component values.

### Lab Procedure:

Build the oscillator circuit you recorded in your notebook in **step 11** of the Pre-Lab.

1. Measure  $V_{OUT_1}$  and  $V_{OUT_2}$  on the scope, and compare the measured results to the simulated results. Are the frequency and duty cycle what you expected? Include images of  $V_{OUT_1}$  and  $V_{OUT_2}$  as a function of time in your notebook.
2. Use the FFT function of the scope to examine the output signals in the frequency domain. Include images of  $V_{OUT_1}$  and  $V_{OUT_2}$  as a function of frequency domain in your notebook.
3. Do you observe both even and odd harmonics in the frequency spectrum? If so, your duty cycle is not 50%. The duty cycle can be adjusted by changing the DC reference voltage that is controlled by the variable resistor. While observing the FFT signal on the scope, adjust the variable resistor to minimize the even harmonics. Determine the reference voltage that minimizes the even harmonics.
4. Because the spice model of the LM741 is only an approximation to the actual opamp, both the oscillation frequency and duty cycle may differ from the specification. If necessary, redesign the oscillator circuit to generate a  $5 \pm 0.2$  kHz output signal with a duty cycle of  $50 \pm 2\%$ . What are the final values of resistors  $R_1$ ,  $R_2$ , and  $R_3$ , and the DC reference voltage at the opamp? Include images of  $V_{OUT_1}$  and  $V_{OUT_2}$ , in both the time domain and the frequency domain, in your notebook.
5. Measure the magnitude of the first five harmonics for both the triangular- and square-wave outputs and compare these results to the theoretical values based on the coefficients of the Fourier series. Record the results in a table in your notebook. Reference this table in your table of contents.

### Post-Lab:

Compare the performance of the simulated design with the actual design. How did the final component values of the actual design compare with the simulated design. Did the simulation provide you with a good prediction of the actual circuit performance?