

**ECE 214 - Lab #10**  
**Thévenin Equivalent Impedance**  
11 April 2022

## Introduction

In this lab, you will examine the Thévenin equivalent output impedance of the DC-DC Power Supply designed and built in [Lab #9](#).

## Pre-Lab

1. For the DC-DC Power Supply of [Lab #9](#), derive the Thévenin equivalent output impedance as a function of frequency. Calculate the Thévenin equivalent impedance for the two operating conditions below.
  - (a) *Condition 1*: switch S1 in the boost converter is closed (the D and S terminals of the transistor are shorted) and switch S2 is open (there is no current through the diode).
  - (b) *Condition 2*: switch S1 in the boost converter is open (the D and S terminals of the transistor are open) and switch S2 is closed (the diode is a short-circuit).
2. Plot the following on semi-log graphs.
  - (a) The magnitude of the Thévenin equivalent output impedance as a function of frequency for frequencies between 1 Hz and 1 MHz for both operating conditions described in [step 1](#).
  - (b) The phase angle of the Thévenin equivalent output impedance as a function of frequency for frequencies between 1 Hz and 1 MHz for both operating conditions described in [step 1](#).
  - (c) The real part of the Thévenin equivalent output impedance as a function of frequency for frequencies between 1 Hz and 1 MHz for both operating conditions described in [step 1](#).
  - (d) The imaginary part of the Thévenin equivalent output impedance as a function of frequency for frequencies between 1 Hz and 1 MHz for both operating conditions described in [step 1](#).

## Lab Procedure

1. For the DC-DC Power Supply of [Lab #9](#), use the impedance analyzer in the Analog Discovery II to measure the Thévenin equivalent output impedance as a function of frequency for the two operating conditions described above.
  - (a) Deactivate the DC supply voltage from [Lab #9](#) by removing the 12 V power brick and replacing it with a short circuit.
  - (b) To create *Condition 1* described in [Pre-Lab step 1a](#), remove the diode from the boost-converter circuit.
  - (c) To create *Condition 2*, replace the diode with a short circuit in the boost-converter circuit. This produces *Condition 2* described in [Pre-Lab step 1b](#).

2. Plot the measured output impedances as described in **Pre-Lab step 2**.

### **Post-Lab**

Compare the calculated and measured Thévenin equivalent output impedance of the power supply. Discuss the results of this analysis in your technical report.