

## ECE 214 - Lab #10 Thévenin Equivalent Circuits

22 April 2019

**Introduction:** In this lab, you will analyze and measure the Thévenin equivalent input impedance and the voltage gain, for both a common emitter amplifier, and a common emitter amplifier with emitter degeneration resistance.

The common emitter amplifier circuit is shown in **Figure 1(a)**. This circuit incorporates a 2N2222 NPN bipolar junction transistor (BJT) for amplification. An equivalent small-signal circuit model is shown in **Figure 1(b)**.

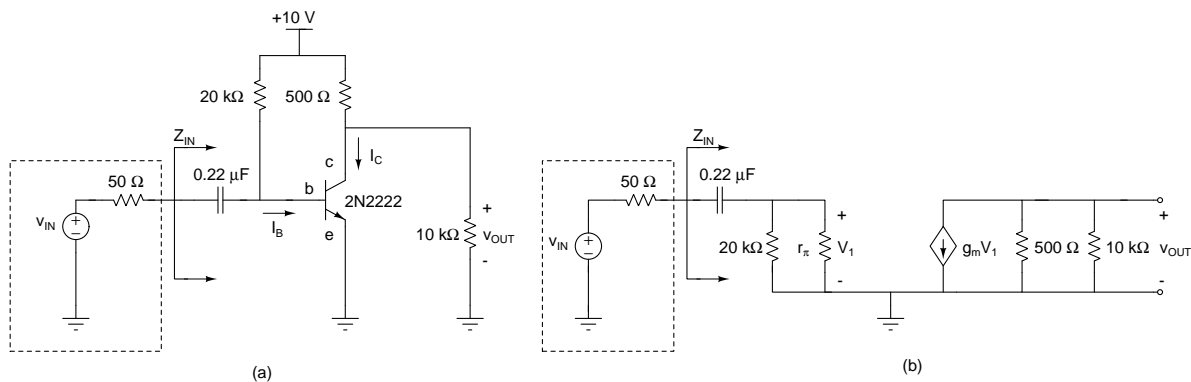


Figure 1: (a) Common emitter amplifier circuit, and (b) equivalent low frequency small-signal circuit model.

A modified common emitter amplifier circuit with emitter degeneration resistance is shown in **Figure 2(a)**. This circuit incorporates a 20 Ω resistor between the emitter and ground. The low frequency equivalent small signal circuit model is shown in **Figure 2(b)**.

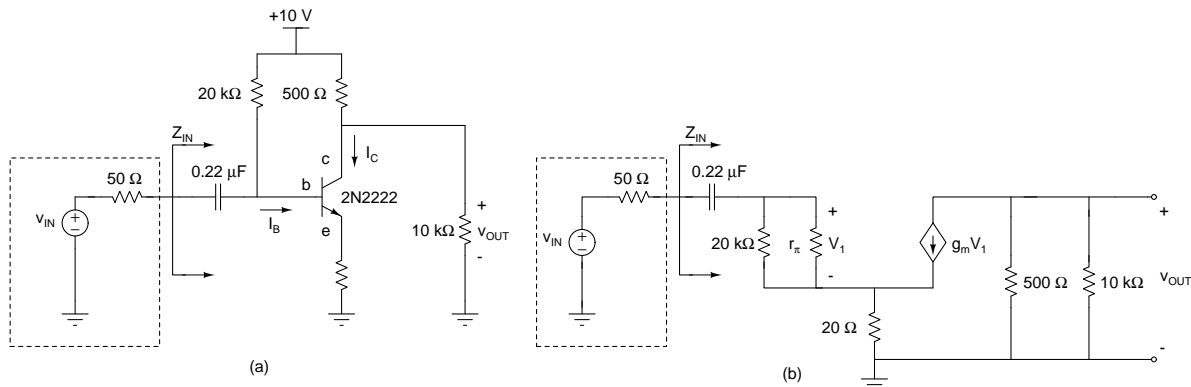


Figure 2: (a) Common emitter amplifier circuit with a 20 Ω emitter degeneration resistor, and (b) equivalent low frequency small-signal circuit model.

### Pre-Lab:

1. For the circuit shown in **Figures 1(b)** and **2(b)**, calculate:

- (a) the voltage gain ( $v_{OUT}/v_{IN}$ ), and
- (b) the Thévenin equivalent input impedance ( $Z_{IN}$ )

in terms of the transistor input resistance ( $r_{\pi}$ ) and transconductance ( $g_m$ ). Assume the input signal has a frequency of 5 kHz. Complete **Table 1** below:

Table 1: Voltage gain and Thévenin input resistance in terms of the parameters  $r_{\pi}$  and  $g_m$ .

	Amplifier (Figure 1)	Amplifier (Figure 2)
$v_{OUT}/v_{IN}$		
$Z_{IN}$		

2. For the circuit in **Figure 1**, devise an experiment to measure the DC currents  $I_C$  and  $I_B$ .

### Lab Procedure:

- 1. Build the circuit shown in **Figure 1**.
- 2. Measure the DC current  $I_C$  in mA. Calculate the transconductance:  $g_m = 38.6 \times I_C$  mA/V.
- 3. Measure the DC current  $I_B$  in mA. Calculate the current gain  $\beta = I_C/I_B$  and  $r_{\pi} = \beta/g_m$  k $\Omega$ .
- 4. Using the values of  $r_{\pi}$  and  $g_m$  determined above, calculate the expected voltage gain and Thévenin equivalent input impedance. Complete **Table 2** below:

Table 2: Expected voltage gain and Thévenin input resistance based on the determined values of  $r_{\pi}$  and  $g_m$ .

	Amplifier (Figure 1)	Amplifier (Figure 2)
$v_{OUT}/v_{IN}$		
$Z_{IN}$		

5. Set input source to generate a sine wave with an amplitude of 20 mV and a frequency of 5 kHz.
6. Measure the voltage gain ( $v_{OUT}/v_{IN}$ ) and Thévenin equivalent input impedance ( $Z_{IN}$ ).
7. Build the circuit shown in **Figure 2**.
8. Measure the voltage gain ( $v_{OUT}/v_{IN}$ ) and Thévenin equivalent input impedance ( $Z_{IN}$ ).
9. Complete **Table 3** below:

Table 3: Measured voltage gain and Thévenin input impedance

	<b>Amplifier (Figure 1)</b>	<b>Amplifier (Figure 2)</b>
$v_{OUT}/v_{IN}$		
$Z_{IN}$		

**Post-Lab:** For the two amplifier circuits, compare the expected voltage gain and Thévenin input impedance to the measured values. Are the small-signal models a good representation of the actual circuits?