

ECE 214 Lab Report

DC-DC Power Supply

Author 1
Author 2

March 19, 2020

Abstract

In the abstract, give the reader a general idea of what the lab and report are about. The abstract should be on your cover page. Highlight the major sections of the circuit without going into too much detail. The abstract should stand alone, meaning that the reader should not have to look at the report itself to get an idea of what the report is about. Additionally, provide one or two of the most important results you obtained in lab. For example, if you built a DC–DC power supply, you would indicate that the power supply had a DC input of 10 V, and produced a DC output of Y V with an ac ripple of xx mV at a fundamental frequency of yy kHz. Some ways to begin the abstract include: “The design and simulation of a [circuit] is described.” On another note, when you list the names of the authors, list them in alphabetical order by last name.

Contents

List of Figures	iv
List of Tables	v
1 Introduction	2
2 Circuit Design and Analysis	2
2.1 Boost Converter Circuit and Analysis	2
2.1.1 Calculation of Energy Loss in the Capacitor	2
2.1.2 Calculation of Time for Current to Flow Into the Inductor	2
2.1.3 Calculation of Time for Current to Flow Out of the Inductor	2
2.1.4 Calculation and Selection of Output Resistor	2
2.1.5 Calculation of Function Generator Settings	2
2.2 Astable Multivibrator Circuit and Analysis	2
2.2.1 Calculation of Frequency and Duty Cycle	2
2.2.2 Selection of Capacitors Values	2
2.3 Low Pass Filter Circuit and Analysis	2
2.4 DC–DC Power Supply Circuit and Analysis	2
2.5 Thévenin Equivalent Output Impedance of DC-DC Power Supply	2
3 Simulated Performance	2
3.1 Boost Converter Simulation	2
3.1.1 Transient Analysis	2
3.1.2 Current Through Transistor	2
3.1.3 Temperature Analysis	2
3.2 Astable Multivibrator Simulation	2
3.2.1 Transient Analysis	2
3.2.2 Capacitor Sensitivity Analysis	2
3.3 Low Pass Filter Simulation	2
3.4 DC-DC Power Supply	2
3.4.1 Transient Simulation	2
3.4.2 Temperature Range of Operation	2
3.4.3 Yield Analysis	2
4 Discussion	2
4.1 Boost Converter	2
4.2 Astable Multivibrator	2
4.3 Low Pass Filter	2
4.4 DC-DC Power Supply	2
5 DC–DC Power Supply Cost Estimate	2
6 Conclusions	2
Appendices	3

A This is the first appendix	3
B This is the second appendix	3
References	4